

11/2/26

Exp: no: - 3

Determination of voltage in circuit using nodal analysis:-


Aim:-

To determine the voltage in the circuit using nodal analysis both theoretically and Practically for a given DC circuit:-

Apparatus Required.

S.L.no	Apparatus	Specification	Quantity
1	Regulated power supply (RPS)	20 - 30V	1
2	Multimeter	— — —	1
3	Resistors	470 Ω , 330 Ω	3, 2
4	Bread board	— — —	1

Circuit diagram:-

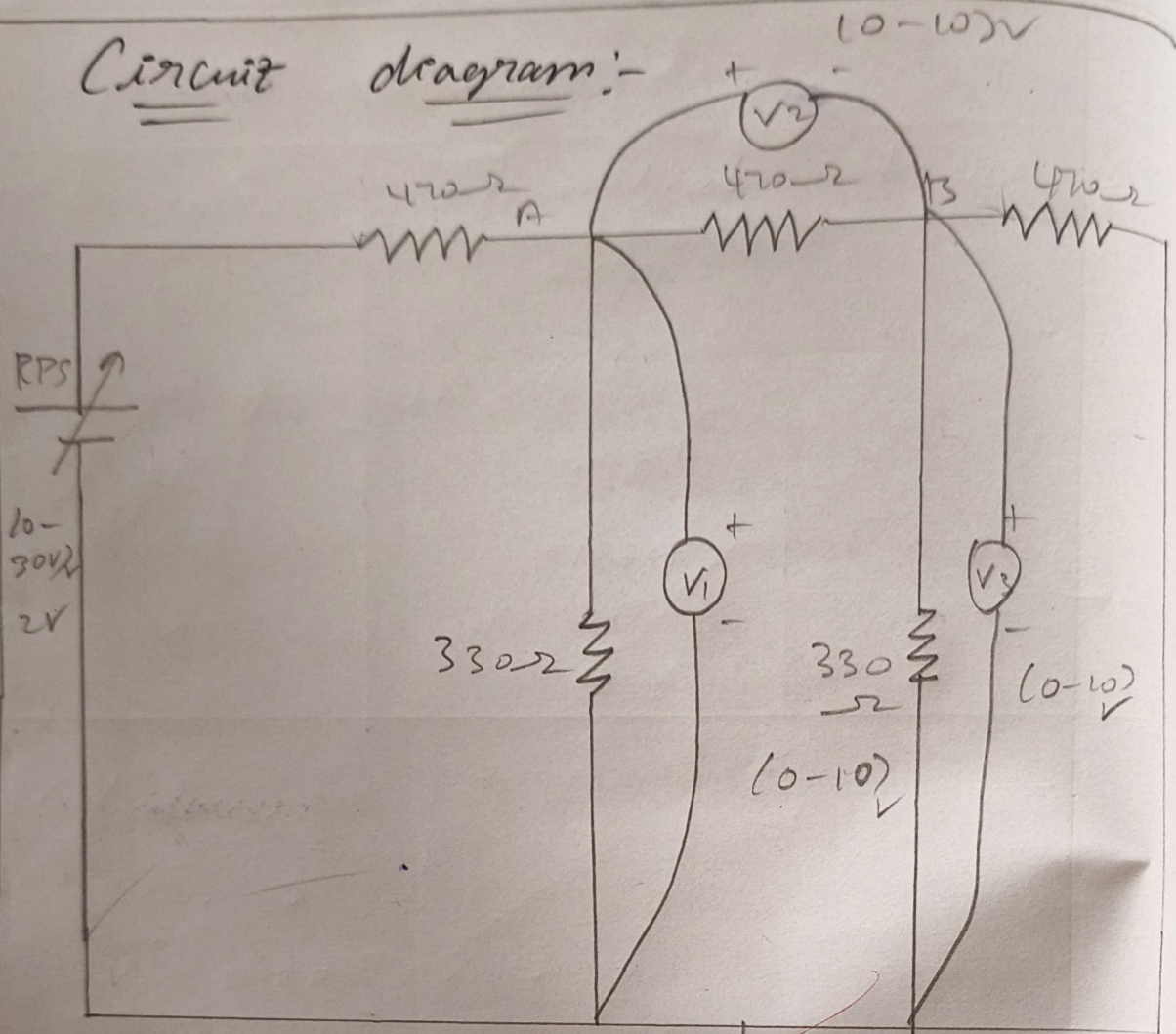

~~Nodal circuit.~~

Result:-
 Thus, the mesh analysis is verified
 Practically and theoretically for nodal
 analysis for 2V & 10V source.
 1) The current across 330Ω resistor is 0.1mA
 2) The current across 470Ω resistor is 0.1mA
 3) The current across 330Ω resistor is 0.1mA

Tabular column:-

Parameter	Theoretical	Practical
2V	0.92	0.98
5V	2.61	2.68
10V	5.39	5.47
14V	7.59	7.66

old verified

Calculations:-

For 2V

$$V_1 = 0.20, \quad V_2 = 0.72$$

$$V = V_1 + V_2$$

$$V = 0.92V$$

For 5V

$$V_1 = 0.60, \quad V_2 = 2.09$$

$$V = V_1 + V_2$$

$$V = 0.60 + 2.09$$

Procedure :-

- 2). Give connections as per the circuit diagram.
- 3). Switch on the supply, vary the RPS (Regulated power supply) and set a particular input voltage.
- 4). Note down the readings of ammeter and voltmeters and tabulate them.
- 5). Vary the RPS for different input voltages and note down the readings of all the meters.
- 6). Reduce the RPS to its minimum value and switch off the supply.
- 7). Using the tabulated values, verify Kirchoff's law practically and verify it theoretically.

$$V = 2.61V$$

For 10V

$$V_1 = 1.30, \quad V_2 = 4.09$$

$$V = V_1 + V_2$$

$$V = 5.39V$$

For 14V

$$V_1 = 1.81, \quad V_2 = 5.78$$

$$V = V_1 + V_2$$

$$V = 1.82 + 5.78$$

$$V = 7.59V$$

Marks Split -up:-

Sl. no	Description	Marks allotted	Marks obtained.
1	Experimented Setup / Connections	20 marks	20
2	Observation / Readings	20 marks	20
3	Calculations / Results	20 marks	10 10
4	Viva	20 marks	20
5	Theoretical	20 marks	
		Total	80

Result:-

② Thus, the nodal analysis is verified practically and theoretically. The resultant voltages for $\underline{2V}$ supply are:-

- a) The voltage V_1 is 0.96 V.
- b) The voltage V_2 is 2.68 V
- c) The voltage V_3 is 5.47 V
- d) The voltage V_4 is 7.66 V.